

FRONT END

Corrections

28 JULY 2004

- 1 Remember the corrections that must be done on the solder side of the board.
- 2 RFC10 is not on the schematic or the parts list. Should also be approx. 1 uH.
- 3 C68 and C69 has no ground connection on the board. Must be done. C68 is SMD
- 4 Roofing circuitry, a few changes have been done on my board. These changes could be caused the deviating parameters of the x-tals (I guess). The corrections were all done with the purpose of getting the filter curve to look good-meaning low inserting loss, minimum ripple and symmetrical with an acceptable bandwidth.

A C112 and C95 are now in the range of 68-78pF.

B C117 and C90 are now appr. 22pF.

After these modifications have been done, the results are shown on the following pages.

- 5 During the testing of the frontend board I found that the relay RLY2A had the coil reversed. The + end of the coil should in fact go to +12V and not to the ULN2803.
RLY2's + end should also go to +12V and not to pin 18 of the ULN2803.
Now I got the relays to activate - but in a wrong way. The track to pin 16 should go to pin 17 and the track to pin 17 should go to pin 16.
Doing this means that the displayed attenuation 0-6-12-18 dB and S-meter readings now works.



A lot of measurements have been done on the roofing filter. I was not satisfied with the symmetry and the ripple. Trying to change values was not a success. It seems difficult to adjust in general. I did not measure the x-tals, so I do not know how accurate they are. I assume they are not of the highest quality.


One trick that – for me – solved all problems was to eliminate the x-tal Co (or most of it) by means of a choke and then adjust the capacitors. Now it is possible to change everything. The center frequency, the passband and the ripple can now - with some patience - be adjusted to optimum for both channels. The chokes I used were 68uH from Farnell (513-519). I tried other chokes, but this one worked ufb. The chokes were soldered directly across every x-tal .


The values I have found may not be optimum with your x-tals To adjust the filter it is a must to have a good and accurate networks tester. I am using the networks tester that was described in FunkAmateur a few years back. (Or you could use the N2PK VNA).

See “measured response” below.....

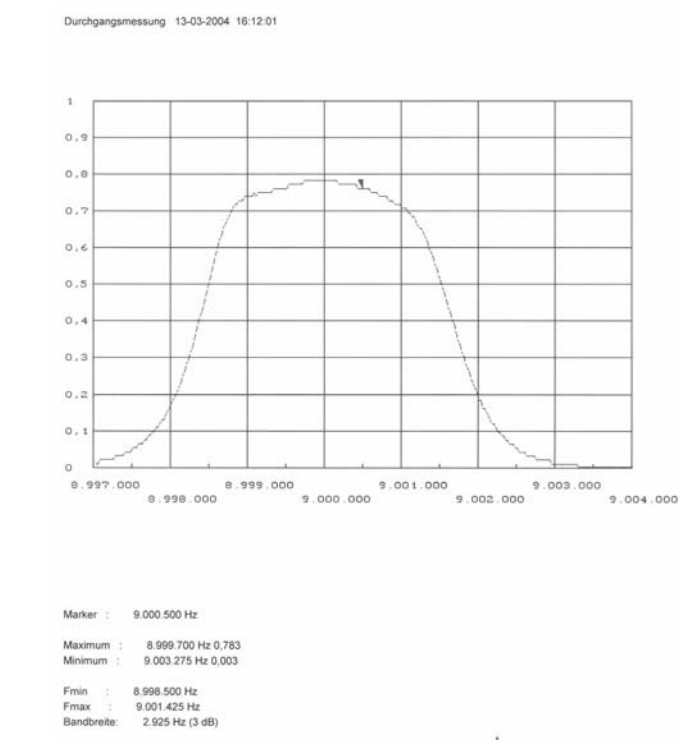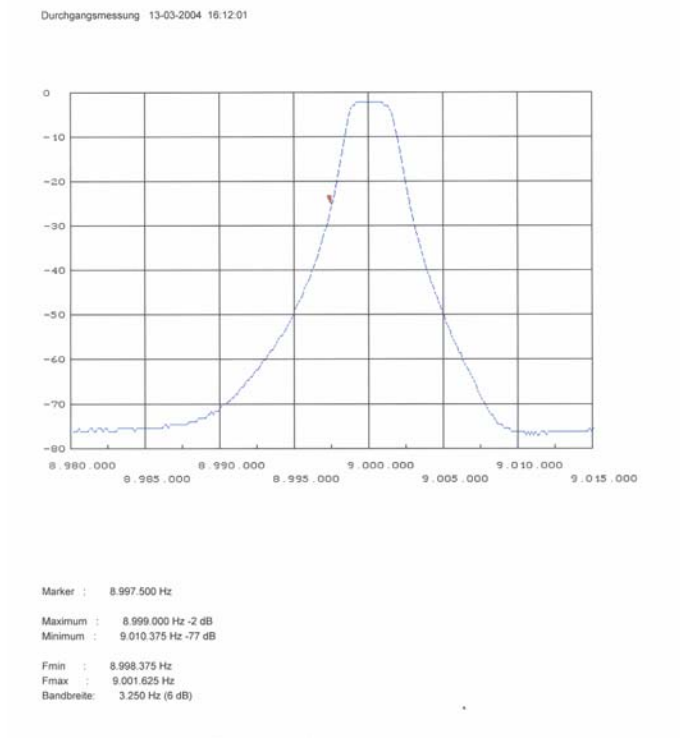Measured response (OZ9FW) through the Combiner + Roofing filter + Combiner
 Top picture log vertical scale – Bottom picture linear scale!





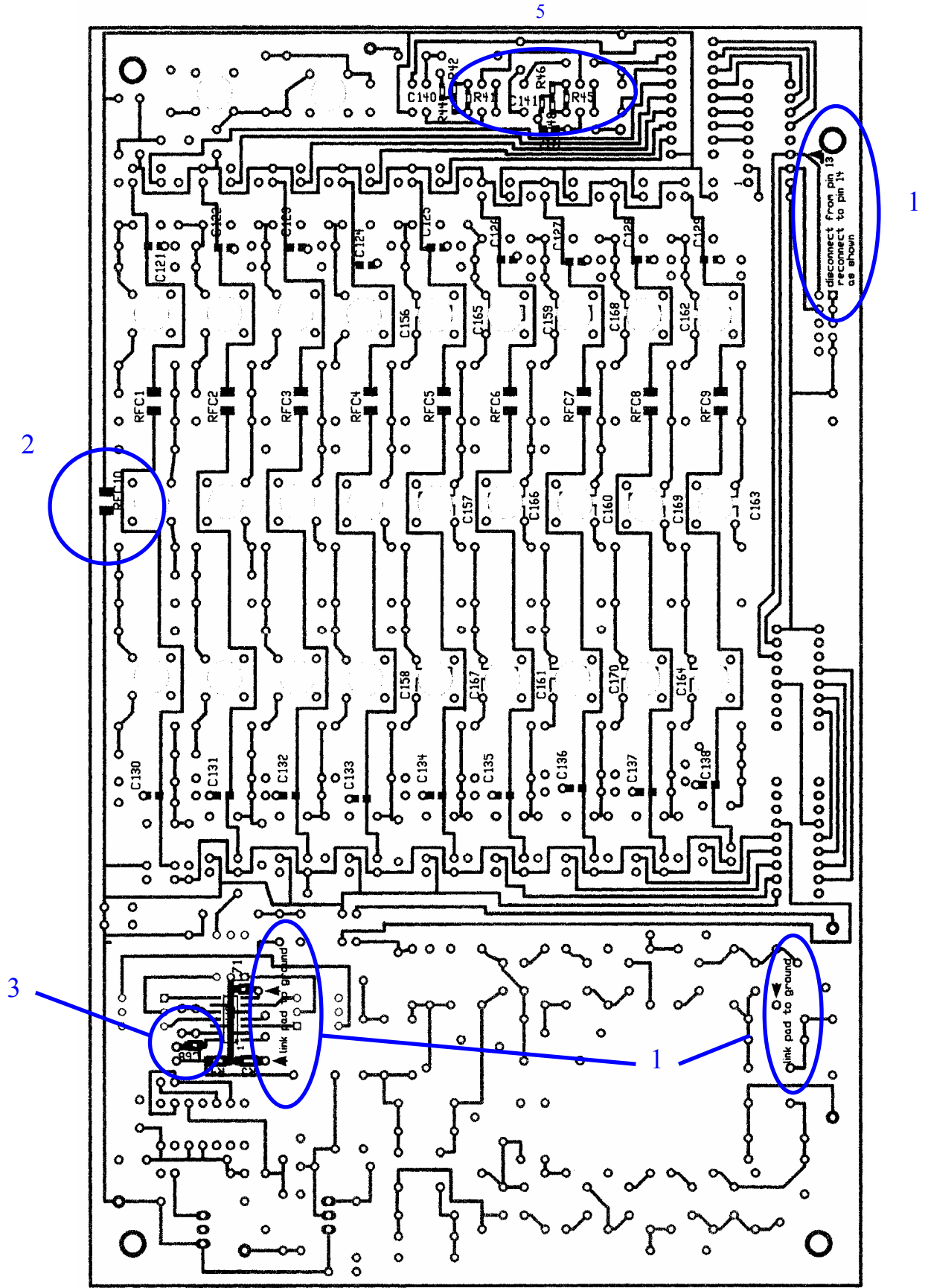

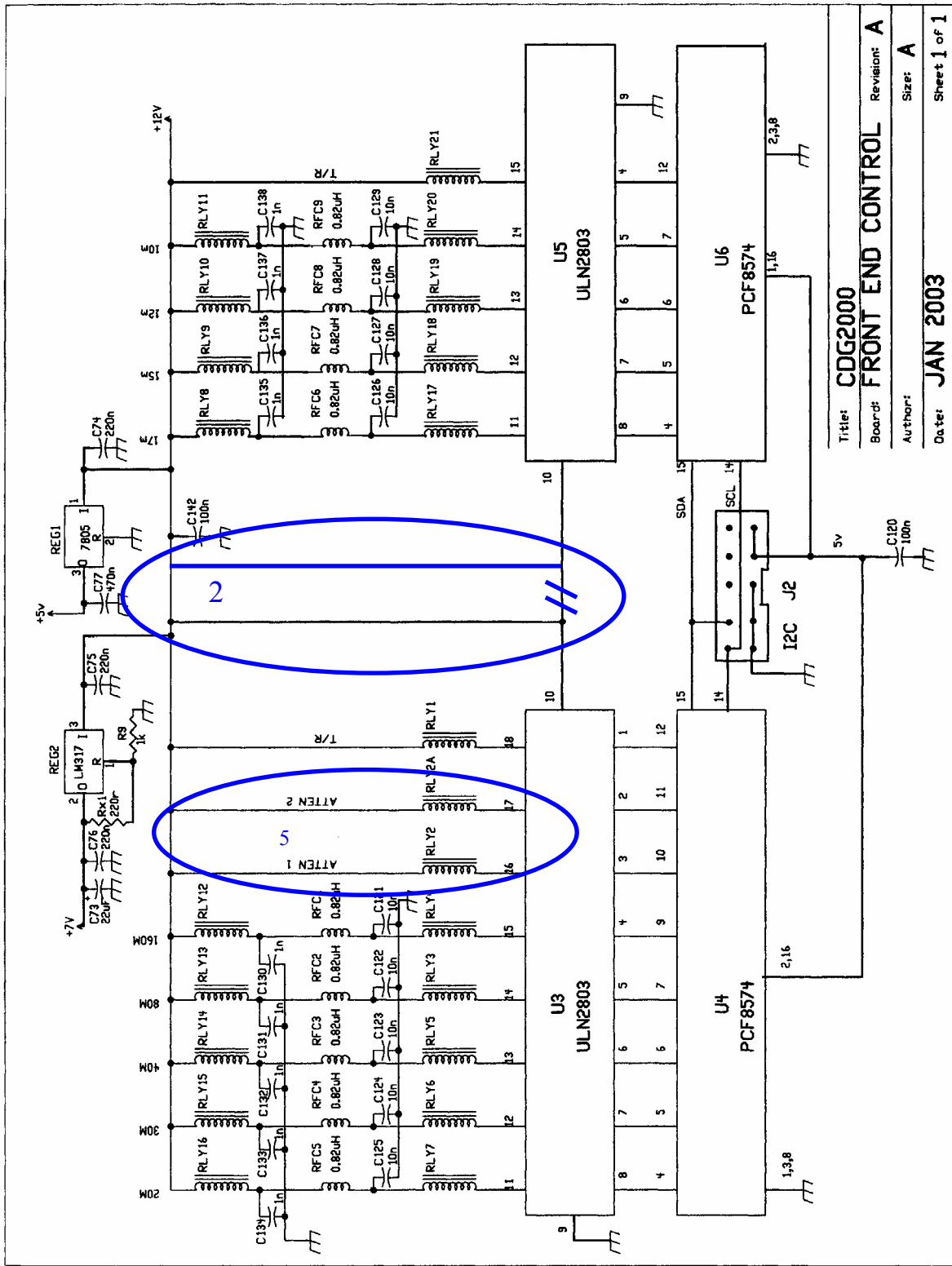



Title: **CDG2000**
 Board: **FRONT END CONTROL** Revision: **A**
 Author: **A** Size: **A**
 Date: **JAN 2003** Sheet 1 of 1

12 and 10m BAND PASS FILTERS

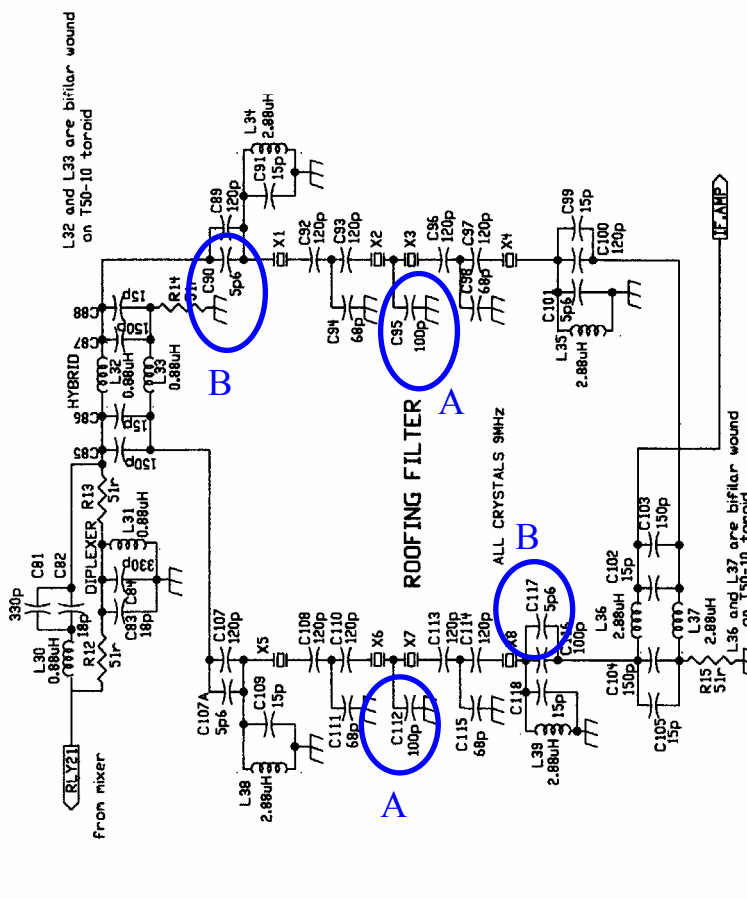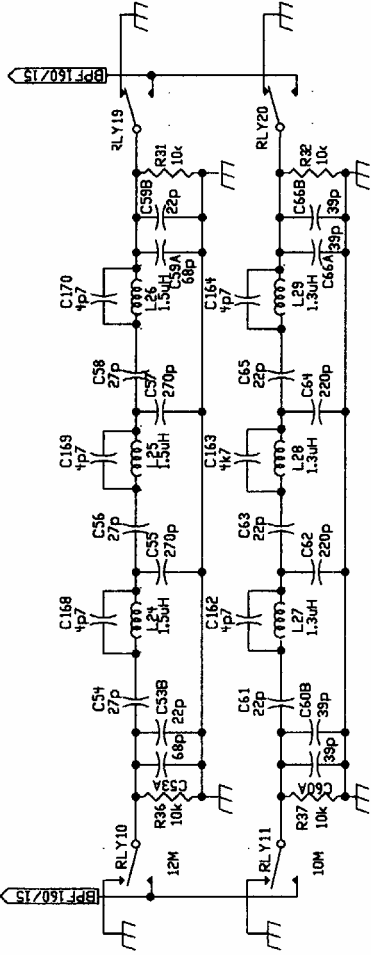

Title:	CDG2000	Revision:	A
Board:	FRONT END PART 3	Author:	A
Date:	JAN 2003	Sheet	1 of 1

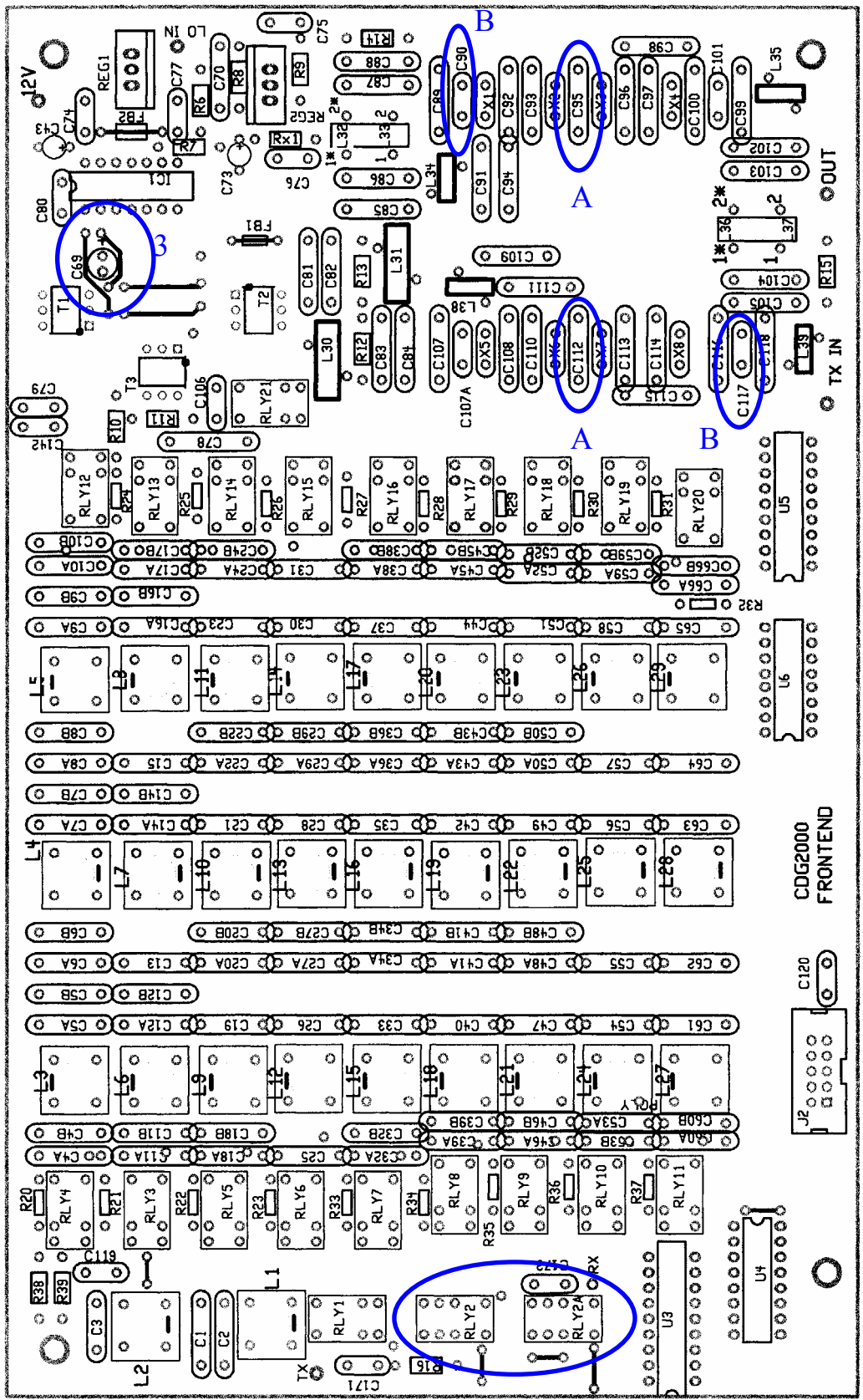

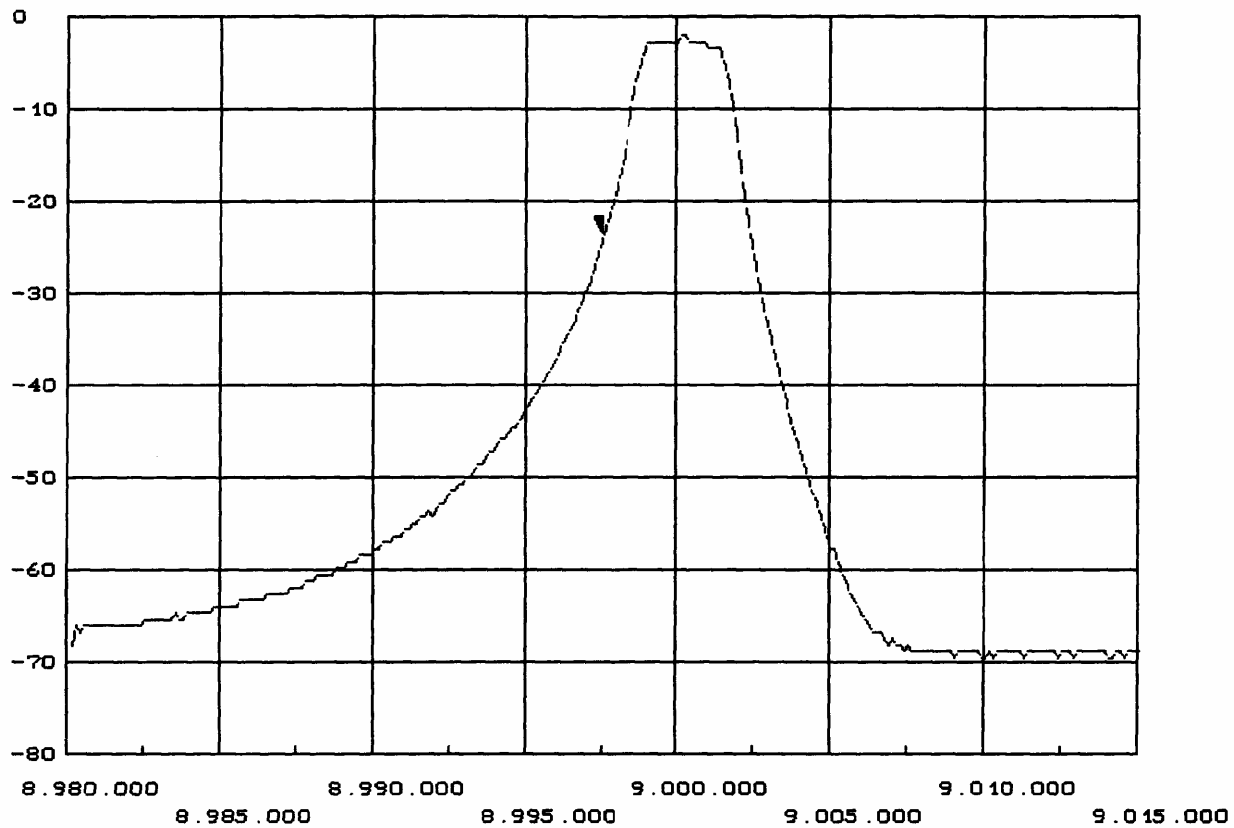

Marker : 8.997.500 Hz

Maximum : 9.000.000 Hz -2 dB


Minimum : 9.008.875 Hz -70 dB

Fmin : 8.998.500 Hz

Fmax : 9.001.625 Hz

Bandbreite: 3.125 Hz (6 dB)

Durchgangsmessung 29-04-2003 07:23:46

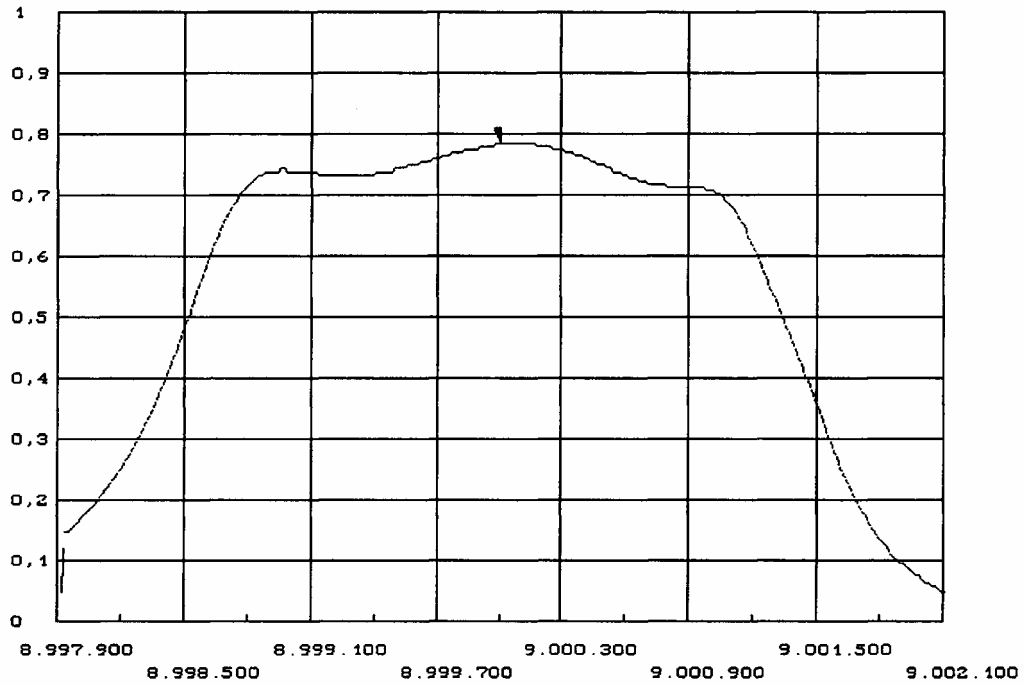

Marker : 9.000.000 Hz

Maximum : 8.999.955 Hz 0,785


Minimum : 8.997.900 Hz 0,048

Fmin : 8.998.545 Hz

Fmax : 9.001.260 Hz

Bandbreite: 2.715 Hz (3 dB)

Durchgangsmessung 28-04-2003 18:17:09

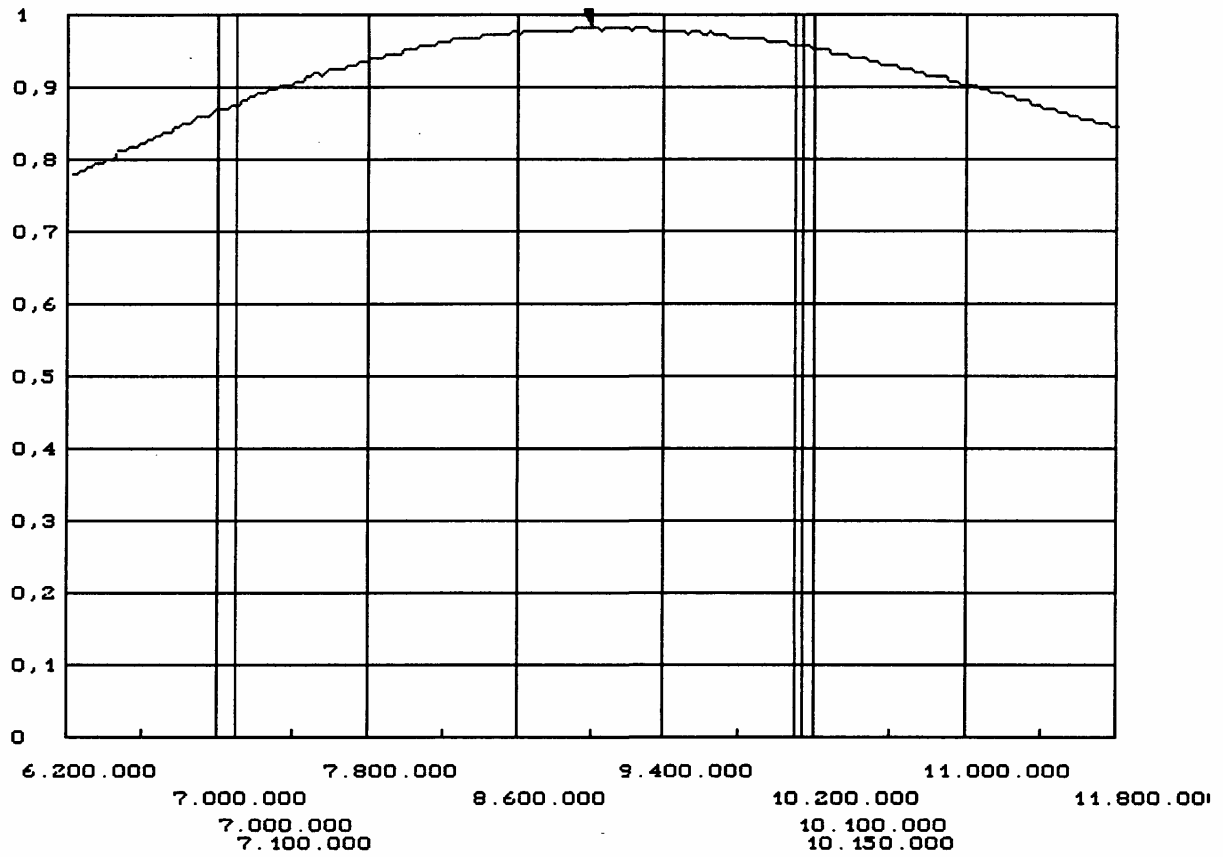

Marker : 9.000.000 Hz

Maximum : 8.880.000 Hz 0,983

Minimum : 6.200.000 Hz 0,780

Fmin :

Fmax :

Bandbreite: